

TRANSCEIVER CW F8EOZ - Audio Amplifier - Darlington pair stage - V 30/12/2012 12:40

--- Operating Point ---

```

V(vcc):      13.8      voltage
V(p):       1.48705      voltage
V(db):       1.48705      voltage
V(de):      0.278174      voltage
V(dc):      10.9866      voltage
V(eg):        0      voltage
V(af_in):   7.43527e-017      voltage
V(af_out):  5.16371e-013      voltage
I(C3):     9.49957e-020      device_current
I(C2):     5.16371e-016      device_current
I(C1):     1.48705e-018      device_current
I(C):      1.30742e-017      device_current
I(Rg):    -1.48705e-018      device_current
I(Rload):  5.16371e-016      device_current
I(R2):     0.00281338      device_current
I(R1):     3.16652e-005      device_current
I(Re):     0.00278174      device_current
I(Rv1a):   3.16397e-005      device_current
I(Rv1b):   3.16394e-005      device_current
I(V2):     1.48705e-018      device_current
I(V1):    -0.00281338      device_current
Ix(q1:C):  0.00278171      subckt_current
Ix(q1:B):  2.56506e-008      subckt_current
Ix(q1:E): -0.00278174      subckt_current

```

